

Activity 1


September 5, 2020

1 Activity 1

Class activity. Solve for current.

1.0.1 Problem 1

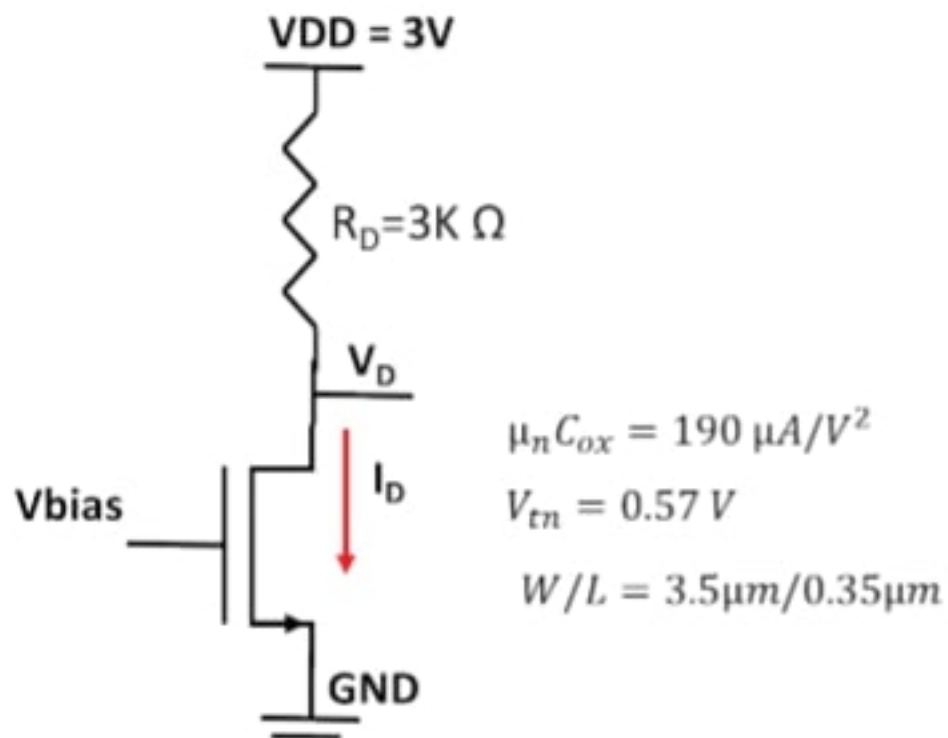Q1: For the circuit below, fill in Table 1



V_{bias}	MOSFET Operation Mode	I_D (mA)	V_D (V)
0.5	OFF	0	3
1.0	SAT	.175	2.47

V_{bias}	MOSFET Operation Mode	I_D (mA)	V_D (V)
1.2	SAT	.377	1.87
1.5	SAT	.77	.69
2.0	LINEAR	.87	.37
3.0	LINEAR	.93	.21

```
[49]: import cmath

# saturation
def saturation_current (VGS, VTH, K,fet_mode=""):
    if fet_mode=="sat":
        print("The saturation current is: {} mA".format(0.5*K*(VGS-VTH)**2*10**3))
        return 0.5*K*(VGS-VTH)**2
    return None

def drain_voltage (VCC=None, ID=None, RD=None, VGS=None, VTH=None, VDS=None, fet_mode=''):
    if fet_mode=="sat":
        VDS = round(VCC-ID*RD,3)
        mode_true = VDS > (VGS-VTH)
        print("VDS = {} V, the assumption is {}".format(VDS, mode_true))
        return VDS
    elif fet_mode=="triode":
        mode_true = VDS < (VGS-VTH)
        print("VDS = {} V, the assumption is {}".format(VDS, mode_true))
        return VDS
    return None

# Triode
def quadratic_formula (a,b,c):
    d = (b**2) - (4*a*c)
    sol1 = (-b-cmath.sqrt(d))/(2*a)
    sol2 = (-b+cmath.sqrt(d))/(2*a)
    print('The solution are {0} and {1}'.format(sol1,sol2))
    return [sol1, sol2]

def current_post_quad (VCC, VDS, RD):
    ID = (VCC-VDS)/RD
    print('ID = {} A'.format((VCC-VDS)/RD))
    return ID
```

```
[50]: W = 3.5
L = 0.35
K_prime = 190*10**(-6)
Kn = W/L*K_prime
VGS = 1
VTH = 0.57
```

```

ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
VCC = 3
RD=3000
#verification
drain_voltage (VCC=VCC, ID=ID, RD=RD, VGS=VGS,VTH=VTH, fet_mode='sat')

```

The saturation current is: 0.175655 mA
VDS = 2.473 V, the assumption is True.

[50]: 2.473

```

[51]: W = 3.5
      L = 0.35
      K_prime = 190*10**(-6)
      Kn = W/L*K_prime
      VGS = 1.2
      VTH = 0.57
      ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
      VCC = 3
      RD=3000
      #verification
      drain_voltage (VCC=VCC, ID=ID, RD=RD, VGS=VGS,VTH=VTH, fet_mode='sat')

```

The saturation current is: 0.377055 mA
VDS = 1.869 V, the assumption is True.

[51]: 1.869

```

[52]: W = 3.5
      L = 0.35
      K_prime = 190*10**(-6)
      Kn = W/L*K_prime
      VGS = 1.5
      VTH = 0.57
      ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
      VCC = 3
      RD=3000
      #verification
      drain_voltage (VCC=VCC, ID=ID, RD=RD, VGS=VGS,VTH=VTH, fet_mode='sat')

      # verification fail -> so it's triode
      # VDS
      a = Kn/2
      b = -1*(1/RD+Kn*(VGS-VTH))
      c = VCC/RD
      Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)
      VDS = min(abs(Vd1),abs(Vd2))

```

```
print('The valid VDS here is: {} V'.format(VDS))
# ID
ID = current_post_quad(VCC=VCC, VDS=VDS, RD=RD)
```

The saturation current is: 0.821655 mA
VDS = 0.535 V, the assumption is False.
The solution are (0.6939013422053886+0j) and (1.5169758507770679+0j)
The valid VDS here is: 0.6939013422053886 V
ID = 0.0007686995525982037 A

```
[53]: # input parameter
VCC = 3
RD=3000
W = 3.5
L = 0.35
K_prime = 190*10**(-6)
Kn = W/L*K_prime
VGS = 2
VTH = 0.57

# assumption 1: saturation
ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
# verification for saturation
drain_voltage (VCC=VCC, ID=ID, RD=RD, VGS=VGS,VTH=VTH, fet_mode='sat')

# assumption 2: triode
# Solving for VDS
a = Kn/2
b = -1*(1/RD+Kn*(VGS-VTH))
c = VCC/RD
Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)
VDS = min(abs(Vd1),abs(Vd2))
print('The valid VDS here is: {} V'.format(VDS))
# Solving for ID
ID = current_post_quad(VCC=VCC, VDS=VDS, RD=RD)
# verification for triode
VDS = drain_voltage(VDS=VDS, VGS=VGS, VTH=VTH, fet_mode="triode")
```

The saturation current is: 1.9426550000000005 mA
VDS = -2.828 V, the assumption is False.
The solution are (0.3706100625820233+0j) and (2.8402671304004334+0j)
The valid VDS here is: 0.3706100625820233 V
ID = 0.0008764633124726589 A
VDS = 0.3706100625820233 V, the assumption is True.

```
[54]: # input parameter
VCC = 3
```

```

RD=3000
W = 3.5
L = 0.35
K_prime = 190*10**(-6)
Kn = W/L*K_prime
VGS = 3
VTH = 0.57

# assumption 1: saturation
ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
# verification for saturation
drain_voltage (VCC=VCC, ID=ID, RD=RD, VGS=VGS,VTH=VTH, fet_mode='sat')

# assumption 2: triode
# Solving for VDS
a = Kn/2
b = -1*(1/RD+Kn*(VGS-VTH))
c = VCC/RD
Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)
VDS = min(abs(Vd1),abs(Vd2))
print('The valid VDS here is: {} V'.format(VDS))
# Solving for ID
ID = current_post_quad(VCC=VCC, VDS=VDS, RD=RD)
# verification for triode
VDS = drain_voltage(VDS=VDS, VGS=VGS, VTH=VTH, fet_mode="triode")

```

The saturation current is: 5.609655 mA
 VDS = -13.829 V, the assumption is False.
 The solution are (0.21051089379563057+0j) and (5.000366299186825+0j)
 The valid VDS here is: 0.21051089379563057 V
 ID = 0.0009298297020681231 A
 VDS = 0.21051089379563057 V, the assumption is True.

```

[55]: # input parameter
VCC = 3
RD=3000
W = 3.5
L = 0.35
K_prime = 190*10**(-6)
Kn = W/L*K_prime
VGS = 3
VTH = 0.57

# assumption 1: saturation
ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
# verification for saturation
drain_voltage (VCC=VCC, ID=ID, RD=RD, VGS=VGS,VTH=VTH, fet_mode='sat')

```

```

# assumption 2: triode
# Solving for VDS
a = Kn/2
b = -1*(1/RD+Kn*(VGS-VTH))
c = VCC/RD
Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)
VDS = min(abs(Vd1),abs(Vd2))
print('The valid VDS here is: {} V'.format(VDS))
# Solving for ID
ID = current_post_quad(VCC=VCC, VDS=VDS, RD=RD)
# verification for triode
VDS = drain_voltage(VDS=VDS, VGS=VGS, VTH=VTH, fet_mode="triode")

```

The saturation current is: 5.609655 mA
 VDS = -13.829 V, the assumption is False.
 The solution are (0.21051089379563057+0j) and (5.000366299186825+0j)
 The valid VDS here is: 0.21051089379563057 V
 ID = 0.0009298297020681231 A
 VDS = 0.21051089379563057 V, the assumption is True.

[56]:

```

# Problem: what is the drain voltage when MOSFET transition from SAT -> TRI?
# AKA: What VDS would be to make that happen?
# unknown: VGS, VDS, ID
# known: VDS = VGS + VTH, device in saturation.

# input parameter
VCC = 3
RD=3000
W = 3.5
L = 0.35
K_prime = 190*10**(-6)
Kn = W/L*K_prime
VTH = 0.57

a = Kn/2
b = 1/RD
c = -VCC/RD
Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)
VDS = abs(Vd2)
print("VDS would be about: {} V".format(Vd2)) #the positive digit one
ID = (VCC - VDS)/RD
print("ID would be about: {} A".format(ID))
VGS = VDS + VTH
print("VGS would be about: {} V".format(VGS))

```

The solution are (-1.216308559592374+0j) and (0.8654313666099176+0j)
 VDS would be about: (0.8654313666099176+0j) V

ID would be about: 0.0007115228777966942 A
VGS would be about: 1.4354313666099174 V


```
[48]: import matplotlib
import matplotlib.pyplot as plt
import numpy as np


# Data for plotting
def plot_point ( t, data, xlabel, ylabel, title):
    fig, ax = plt.subplots()
    ax.plot(t, data)
    ax.set(xlabel=xlabel, ylabel=ylabel,
           title=title)
    ax.grid()
    plt.show()

VGS = [0.5, 1, 1.2, 1.43, 1.5, 2, 3]
ID = [0,.175,.377,0.71,.77,.87,.93]
VD = [3,2.47,1.87,.86,.69,.37,.21]

# ID vs. VGS
plot_point(t=VGS, data=ID, xlabel = 'VG (V)', ylabel = 'Drain Current (mA)',
           title = 'ID vs. VG')

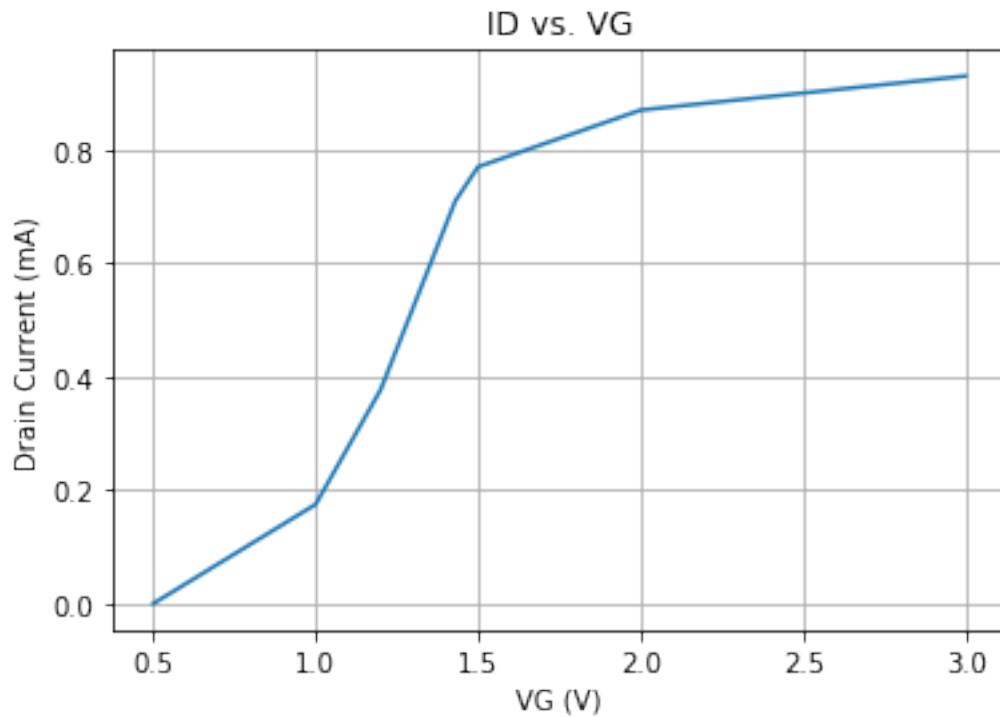
# VD vs. VGS
plot_point(t=VGS, data=VD, xlabel = 'VG (V)', ylabel = 'Drain Voltage (V)',
           title = 'VD vs. VG')
```



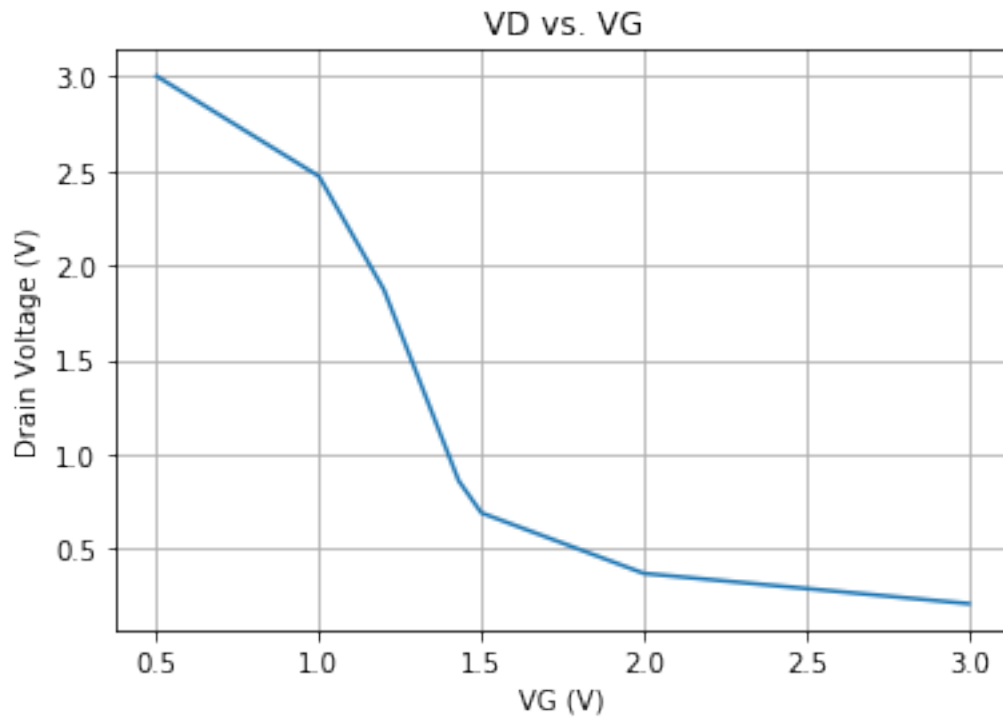

1.0.2 Problem 2

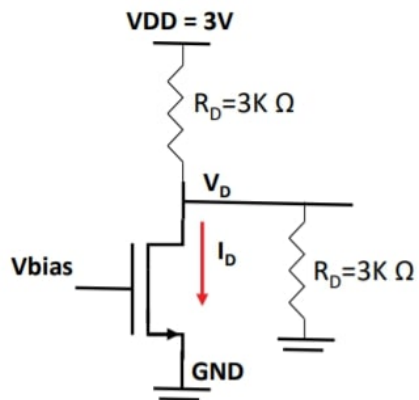Q2: Repeat Q1 for the circuit shown below.



V_{bias}	MOSFET oper. Mode Off/SAT/Linear	I_D (mA)	V_D (V)
0.5V			
1.0V			
1.2V			
1.5V			
2V			
3V			

V_{bias}	MOSFET Operation Mode	I_D (mA)	V_D (V)
0.5	OFF	0	1.5
1.0	SAT	.175	1.23
1.2	SAT	.377	.93
1.5	LINEAR	.650	.514
2.0	LINEAR	.783	.325
3.0	LINEAR	.869	.196

```
[58]: import numpy as np

# Saturation
def drain_voltage (VCC=None, ID=None, RD1=None, RD2=None, VGS=None, VTH=None,
    →VDS=None, fet_mode=''):
    if fet_mode=="sat":
        VDS = parallel_resistance(R1=RD1, R2=RD2)*(VCC/RD1-ID)
        mode_true = VDS > (VGS-VTH)
        print("VDS = {} V, the assumption is {}".format(VDS, mode_true))
        return VDS
    elif fet_mode=='triode':
        mode_true = VDS < (VGS-VTH)
        print("VDS = {} V, the assumption is {}".format(VDS, mode_true))
        return VDS
    return None
def parallel_resistance (R1, R2):
    return R1*R2/(R1+R2)

# Triode
def quadratic_formula (a,b,c):
    d = (b**2) - (4*a*c)
    sol1 = (-b-cmath.sqrt(d))/(2*a)
    sol2 = (-b+cmath.sqrt(d))/(2*a)
    print('The solution are {0} and {1}'.format(sol1,sol2))
    return [sol1, sol2]
def current_post_quad (VCC, VDS, RD1,RD2):
    ID = VCC/RD1-VDS*(parallel_resistance(R1=RD1,R2=RD2)**(-1))
    print('ID = {} A'.format(ID))
    return ID
```

```
[42]: W = 3.5
L = 0.35
K_prime = 190*10**(-6)
Kn = W/L*K_prime
VGS = 1
VTH = 0.57
ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
VCC = 3
```

```
RD=3000
#verification
drain_voltage (VCC=VCC, ID=ID, RD1=RD, RD2=RD,\
                VGS=VGS,VTH=VTH, fet_mode='sat')
```

The saturation current is: 0.175655 mA
VDS = 1.2365175 V, the assumption is True.

[42]: 1.2365175

```
[43]: W = 3.5
      L = 0.35
      K_prime = 190*10**(-6)
      Kn = W/L*K_prime
      VGS = 1.2
      VTH = 0.57
      ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
      VCC = 3
      RD=3000
      #verification
      drain_voltage (VCC=VCC, ID=ID, RD1=RD, RD2=RD,\
                      VGS=VGS,VTH=VTH, fet_mode='sat')
```

The saturation current is: 0.377055 mA
VDS = 0.9344174999999999 V, the assumption is True.

[43]: 0.9344174999999999

```
[38]: W = 3.5
      L = 0.35
      K_prime = 190*10**(-6)
      Kn = W/L*K_prime
      VGS = 1.5
      VTH = 0.57
      ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
      VCC = 3
      RD1=3000
      RD2=3000
      #verification
      drain_voltage (VCC=VCC, ID=ID, RD1=RD, RD2=RD,\
                      VGS=VGS,VTH=VTH, fet_mode='sat')

      # verification fail -> so it's triode
      # VDS
      a = Kn/2
      b = -1*(Kn*(VGS-VTH)+parallel_resistance(R1=RD1, R2=RD2)**(-1))
      c = VCC/RD1
```

```

Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)
VDS = min(abs(Vd1),abs(Vd2))
print('The valid VDS here is: {} V'.format(VDS))
# ID
ID = current_post_quad(VCC=VCC, VDS=VDS, RD1=RD1,RD2=RD2)

```

The saturation current is: 0.821655 mA
 VDS = 0.2675175 V, the assumption is False.
 The solution are (0.5140559592159103+0j) and (2.047698426749002+0j)
 The valid VDS here is: 0.5140559592159103 V
 ID = 0.0006572960271893932 A

```

[39]: W = 3.5
      L = 0.35
      K_prime = 190*10**(-6)
      Kn = W/L*K_prime
      VGS = 2
      VTH = 0.57
      ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
      VCC = 3
      RD1=3000
      RD2=3000
      #verification
      drain_voltage (VCC=VCC, ID=ID, RD1=RD, RD2=RD,\
                      VGS=VGS,VTH=VTH, fet_mode='sat')

      # verification fail -> so it's triode
      # VDS
      a = Kn/2
      b = -1*(Kn*(VGS-VTH)+parallel_resistance(R1=RD1, R2=RD2)**(-1))
      c = VCC/RD1
      Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)
      VDS = min(abs(Vd1),abs(Vd2))
      print('The valid VDS here is: {} V'.format(VDS))
      # ID
      ID = current_post_quad(VCC=VCC, VDS=VDS, RD1=RD1,RD2=RD2)

```

The saturation current is: 1.9426550000000005 mA
 VDS = -1.4139825000000006 V, the assumption is False.
 The solution are (0.3252357544620683+0j) and (3.236518631502844+0j)
 The valid VDS here is: 0.3252357544620683 V
 ID = 0.0007831761636919545 A

```

[40]: W = 3.5
      L = 0.35
      K_prime = 190*10**(-6)
      Kn = W/L*K_prime

```

```

VGS = 3
VTH = 0.57
ID = saturation_current(VGS,VTH,Kn,fet_mode='sat')
VCC = 3
RD1=3000
RD2=3000
#verification
drain_voltage (VCC=VCC, ID=ID, RD1=RD, RD2=RD,\
               VGS=VGS,VTH=VTH, fet_mode='sat')

# verification fail -> so it's triode
# VDS
a = Kn/2
b = -1*(Kn*(VGS-VTH)+parallel_resistance(R1=RD1, R2=RD2)**(-1))
c = VCC/RD1
Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)
VDS = min(abs(Vd1),abs(Vd2))
print('The valid VDS here is: {} V'.format(VDS))
# ID
ID = current_post_quad(VCC=VCC, VDS=VDS, RD1=RD1,RD2=RD2)

```

The saturation current is: 5.609655 mA

VDS = -6.9144825 V, the assumption is False.

The solution are (0.19618255270043303+0j) and (5.365571833264481+0j)

The valid VDS here is: 0.19618255270043303 V

ID = 0.0008692116315330447 A

```

[62]: # Problem: what is the drain voltage when MOSFET transition from SAT -> TRI?
# AKA: What VDS would be to make that happen?
# unknown: VGS, VDS, ID
# known: VDS = VGS + VTH, device in saturation.

# input parameter
VCC = 3
RD1=3000
RD2=3000
W = 3.5
L = 0.35
K_prime = 190*10**(-6)
Kn = W/L*K_prime
VTH = 0.57
print("Find the point where device transition from saturation to linear_\
      ↪region\n")
a = Kn/2
b = parallel_resistance(R1=RD1, R2=RD2)**(-1)
c = -VCC/RD1
print("This is the 2 possible VD value")

```

```

Vd1, Vd2 = quadratic_formula(a=a,b=b,c=c)

#answer
VDS = abs(Vd2)
print("This is the ID value from the valid VDS value")
ID = current_post_quad(VCC=VCC, VDS=VDS, RD1=RD1,RD2=RD2)
VGS = VDS + VTH

#output
print("VDS would be about: {} V".format(Vd2)) #the positive digit one
print("ID would be about: {} A".format(ID))
print("VGS would be about: {} V".format(VGS))

```

Find the point where device transition from saturation to linear region

This is the 2 possible VD value

The solution are (-1.4351955887973646+0j) and (0.7334412028324524+0j)

This is the ID value from the valid VDS value

ID = 0.0005110391981116984 A

VDS would be about: (0.7334412028324524+0j) V

ID would be about: 0.0005110391981116984 A



VGS would be about: 1.3034412028324525 V

```


[47]: VGS = [0.5, 1, 1.2, 1.303, 1.5, 2, 3]
      ID = [0,.175,.377,0.511,.65,.783,.869]
      VD = [1.5,1.23,0.93,.733,.51,.325,.196]

# ID vs. VGS
plot_point(t=VGS, data=ID, xlabel = 'VG (V)', ylabel = 'Drain Current (mA)',
→title = 'ID vs. VG')
# VD vs. VGS
plot_point(t=VGS, data=VD, xlabel = 'VG (V)', ylabel = 'Drain Voltage (V)',
→title = 'VD vs. VG')

```

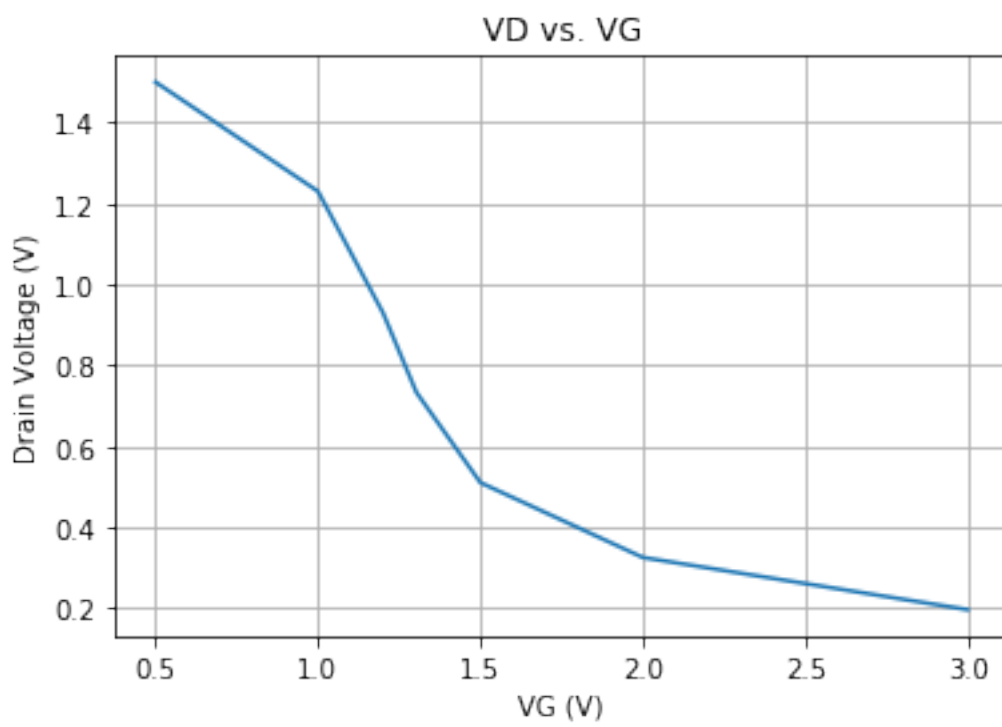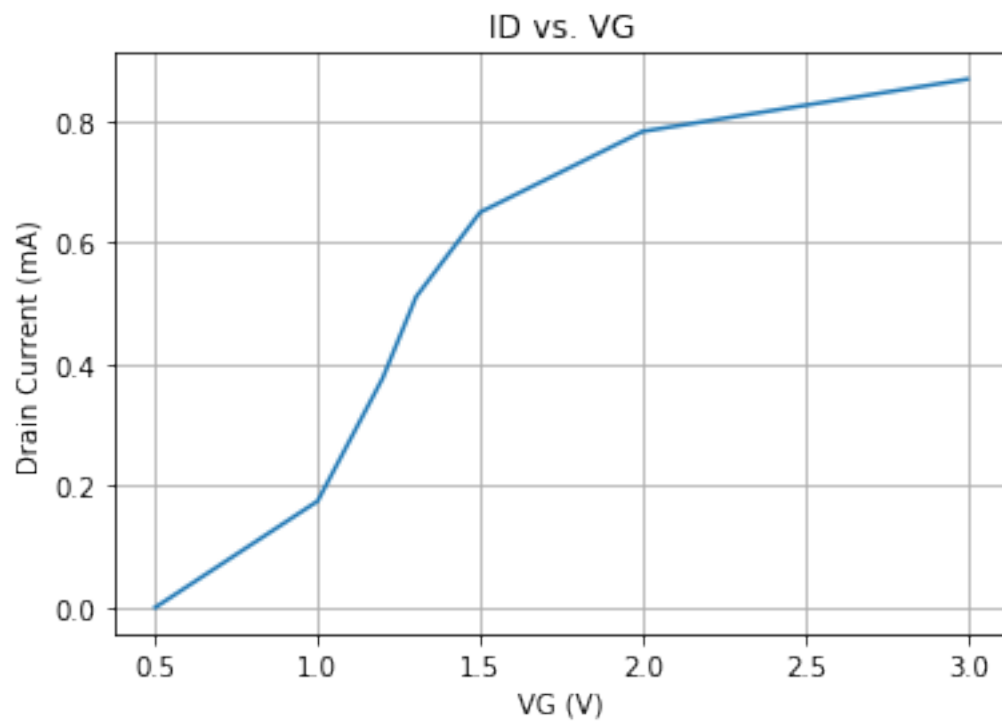


1.0.3 Problem 3

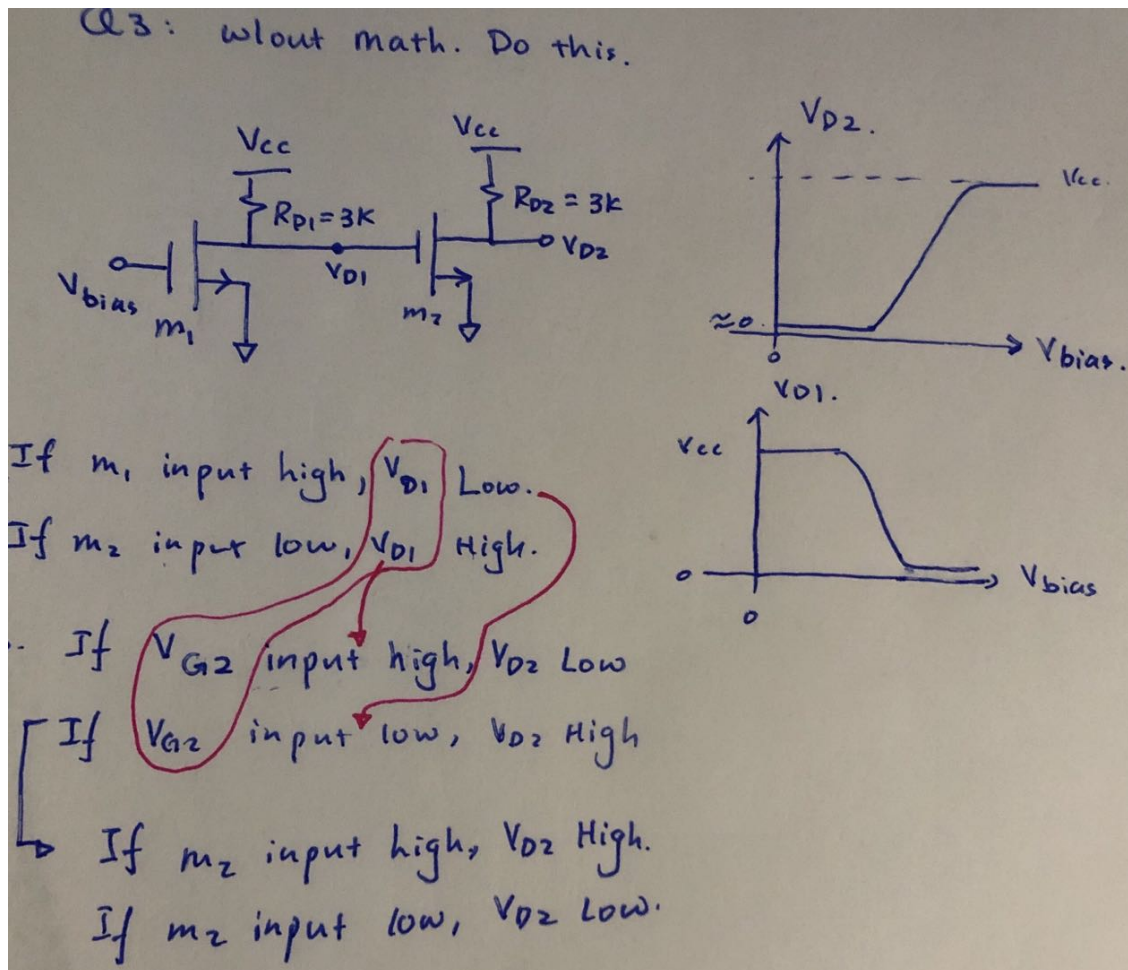

1.0.4 Problem 4, part 1

Q4:

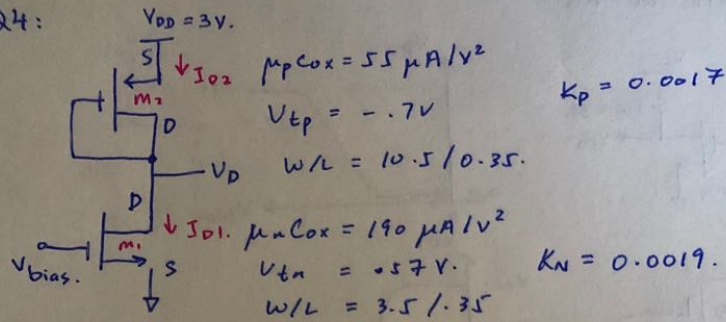

$$V_{bias} = 1V.$$

$$V_{GS} = 1V > V_{tn} \rightarrow \text{ON.}$$

Assume Saturation.

$$I_{D1} = \frac{1}{2} K_n (V_{GS} - V_{tn})^2 \quad I_{D2} = \frac{1}{2} K_p (V_{SG} - |V_{tp}|)^2$$

From m1
from m2.

$\hookrightarrow V_{SG} = V_{CC} - V_D.$

$$I_{D2} = \frac{1}{2} K_p (V_{CC} - V_D - |V_{tp}|)^2$$

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} K_n (V_{GS} - V_{tn})^2 = \frac{1}{2} K_p (V_{CC} - V_D - |V_{tp}|)^2$$

$$\sqrt{\frac{K_n}{K_p}} (V_{GS} - V_{tn}) = V_{CC} - V_D - |V_{tp}|$$

$$V_D = V_{CC} - |V_{tp}| - \sqrt{\frac{K_n}{K_p}} (V_{GS} - V_{tn})$$

$$V_D = 1.845V.$$

$$V_D > V_{GS} - V_{th} \rightarrow \text{True.}$$

1.0.5 Problem 4, part 2

$$I_{D2} = \frac{1}{2} K_p (V_{SG} - |V_{Tp}|)^2 \rightarrow m_2 \text{ sat.}$$

$$I_{D1} = \frac{1}{2} K_n (V_{GS} - V_{tn})^2 \rightarrow m_1 \text{ sat.}$$

$$\frac{1}{2} K_p (V_{SG} - |V_{Tp}|)^2 = \frac{1}{2} K_n (V_{GS} - V_{tn})^2$$

$$\underbrace{V_{SG}}_{m_2} = |V_{Tp}| + \sqrt{\frac{K_n}{K_p}} (\underbrace{V_{GS} - V_{tn}}_{m_1})$$

$$= \boxed{1.15}$$

$$V_{SD} > (V_{SG} - |V_{Tp}|)$$

$$V_{CC} - V_D > V_{SG} - |V_{Tp}|$$

$$V_D < V_{CC} - \boxed{V_{SG}} + |V_{Tp}|$$

$$V_D < 3 - \boxed{1.15} + |V_{Tp}|$$


$$\boxed{V_D < 2.2V}$$

if $m_2 \rightarrow \text{sat}$

$m_1 \rightarrow \text{sat.}$

1.0.6 Problem 5

Q5 :

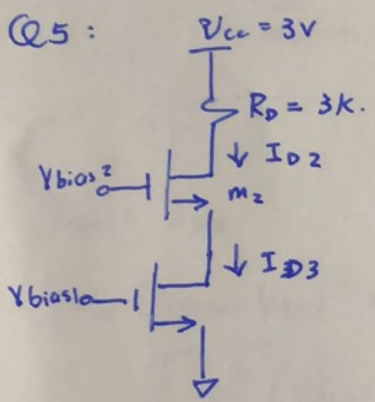

$V_{cc} = 3V$
 $R_D = 3k.$
 $V_{bias1} = 1$
 V_{bias2}
 I_{D2}
 m_2
 I_{D3}

We know $V_{bias1} = 1$ We don't know V_{bias2} .
 To have m_2 in saturation.
 We need $V_{GS} > V_{TH} = 0.57V$
 To have m_2 stay at saturation
 we need $V_{GS} < V_{DS} + V_{TH} = 1.43V$
 $0.57V < V_{GS} = V_{bias2} < 1.43$