


## ECSE 4030 Analog IC Design

### Class Activity – 1 (review on MOSFET biasing, Regions of Operation)

#### Drain current ( $I_D$ ) in the different operating modes for NMOS (NFET) transistor

Off region	$I_D = 0$
Linear Region	$I_D = \mu_n C_{ox} \frac{W}{L} \left( (V_{GS} - V_{tn}) V_{DS} - \frac{1}{2} V_{DS}^2 \right)$ (deep triode) $I_D \approx \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{tn}) V_{DS}$
Saturation Region	$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{tn})^2$
 
#### Q1: For the circuit below, fill in Table 1





$V_{bias}$	MOSFET oper. Mode Off/SAT/Linear	$I_D$ (mA)	$V_D$ (V)
0.5V			
1.0V			
1.2V			
1.5V			
2V			
3V			

Note that by solving KVL, the total voltage  $V_{DD}$  is divided between the voltage drop on the drain resistance and the drop across the drain-source of the transistor such that


$$V_{DD} = V_{DS} + I_D R_D$$

$$V_{DS} = V_{DD} - I_D R_D$$

  --After filling the table, Plot  $I_D$  versus  $V_{bias}$  & plot  $V_D$  versus  $V_{bias}$




 **Q2: Repeat Q1 for the circuit shown below.**



$V_{bias}$	MOSFET oper. Mode Off/SAT/Linear	$I_D(\text{mA})$	$V_D(\text{V})$
0.5V			
1.0V			
1.2V			
1.5V			
2V			
3V			

 Q3: **Without doing the math**, and based on your answer from the previous two questions, what do you expect the voltage at the drain of the second transistor to look like as a function of the bias voltage of the first transistor?




Q4:

Drain current ( $I_D$ ) in the different operating modes for PMOS (PFET) transistor

Off region	$I_D = 0$
Linear Region	$I_D = \mu_p C_{ox} \frac{W}{L} \left( (V_{SG} -  V_{tp} ) V_{SD} - \frac{1}{2} V_{SD}^2 \right)$ (deep triode) $I_D \approx \mu_p C_{ox} \frac{W}{L} (V_{SG} -  V_{tp} ) V_{SD}$
Saturation Region	$I_D = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} -  V_{tp} )^2$

For the circuit shown in Fig. P4(a), find the voltage at the drain  $V_D$  at  $V_{bias} = 1V$ ? **Assume all transistors are in Saturation**

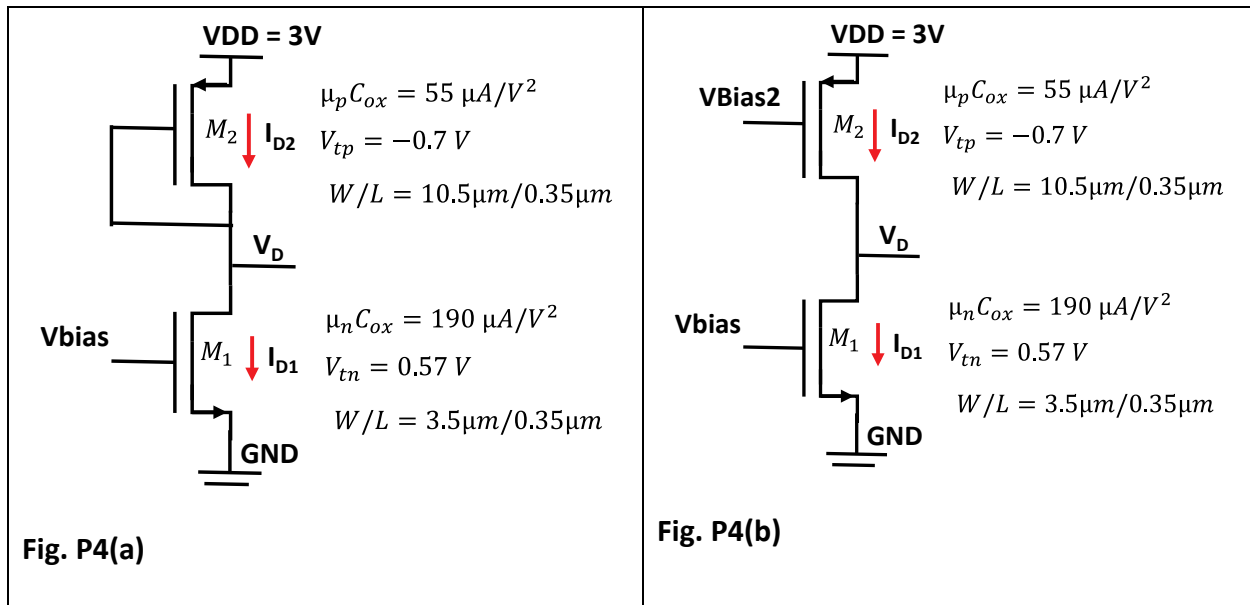If the wire connecting the gate with the drain for transistor  $M_2$  is disconnected as shown in Fig. P4(b), can you still find the voltage  $V_D$



Q5: Something to think about.....

For the circuit shown below, and based on your answer to Q1, Can you guess the value of  $V_{bias2}$  if

$V_{bias1} = 1V$ ? Assume both NMOS transistors are in the saturation region

